

- What are the six level of computers
- [Truth Table]: Define
- [Logic gates]: Define? List them?
 - [Logic Gate 1]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
 - [Logic Gate 2]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
 - [Logic Gate 3]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
 - [Logic Gate 4]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
 - [Logic Gate 5]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
 - [Logic Gate 6]: Explain? Diagram/Symbols/Table/Boolean /Timing Diagram/expression
- Components of logic circuit (7 marks)