

- Six levels of computer include:
  - **Digital logic:** physical implantation of computer circuits (hardware)
  - **Microarchitecture level:** decide which components we use and how we use it
  - **Instructional set architecture level:**

\*Binary operations have 2 inputs unary 1 input. 3 inputs =

- **Truth Table:** describes how logic's circuit output depends on logic level input. Table for all possible input. The convention is exhaust 0 first in input A. Then once all possible combination for input 0. Then raise input
- **Logic gates:** are used to build logic circuits. There are five different types:
  - Or
  - And
  - Not (inverter)
  - Nand
  - Nor
  - Xor
  - Xnor
- **Or gate: + (A + B)**
  - Boolean expression is  $x = A + B$
  - Do first or circuit
- **And Gate: \* (A\*B or AB or Ab)**
  - $X = AB$

- **Not gate: - OR ' (NOTE IF NO A NOT GATE) \*BEFORE TEST RECHECK**
  - Unary only taking one input aka inversion or complementation.
  - Boolean expression:  $X = A$
  
- **Nand gate: negative "AND" (AB with Hat or (AB)')**
  - **2 inputs**
  
  
- **Nor gate: inversion of "or" Bubble represents (A + B with Hat) or (A+B)'**
  
  
  
- **Xor gate:  $A(+ )B$**

- If both input are 1 output is 0
- Mutually exclusive so if both 1 it's not exclusive

- **Xnor gate:** inverted form of xor
  - Opposite of xor

- Boolean is best written as sum of multiple and ie  $y = AB + \bar{A}\bar{B}$
- More efficient is using one type in parallel or series.
- **Multiplexer:** lots of input but only one will be outputted.
- **Decoder:** coded message and you wanted to decode (3 input). All 7 will not be fired only 1.
- **Comparators:** If you have two numbers we use to compare. Someone better (or exclusive or input + output or). If two numbers are equal. If end thing is not 1 then its not equal
- **Shifter:** shift every byte left. Empty spots is zero
- **Half adders:** NOTE:  $1\ 1 = 0$ ,  $0\ 1 = 1$  (sum) (carry 0)
- **Adders:** add circuit or numbers. Carry in is 0/1/0/1

- **Latches (SR):** devices that act as memory cell retain values/write./read. So we can later use it or feedback A gate only uses present input. Store outputs. Based of nor principal. If input s is 1 then output is 0 (opposite of D-latch)
- 
- **Flip Flop:** is latch but are clocked
- **D latch:** difference is that: D (is an input on diagram) = s = R inverse. So if D = 1 then S = 1 R = 0. But if D (input on diagram) = 1 then Q = 1 [Reverse for 0]
- 1 ram = 1 byte

- 5ghz over 2,4ghz is due to carry more bandwidth but attenuated (bounce off walls)
- **Programmable logic arrays:** reduces gate delays keyboard. Contains all gates and combines them.
- **Gate delay:** one is going to turn up before other
- **Clockedspeed** Can't just increase clock speed to increase speed It because you have gate delays to worry about and other factors.

